

(1) おいばいての法則

①向きを含め「を全て大多でおく 一)大多数を一成らしておく。 ②ルプを決め、キルはかり第2

(B)
$$\alpha RI = 3RI_1 \rightarrow I_1 = \frac{\alpha}{3}I$$


$$I,7. (A)I')$$

$$1 = (1-\alpha)RI + (\frac{4}{3}d - \frac{\alpha^2}{3})RI$$

$$= (-\frac{\alpha^2}{3} + \frac{\alpha}{3} + 1)RI$$

$$\int = \frac{1}{\left\{-\frac{1}{3}(\alpha - \frac{1}{2})^{2} + \frac{13}{12}\right\} \mathbb{R}}$$
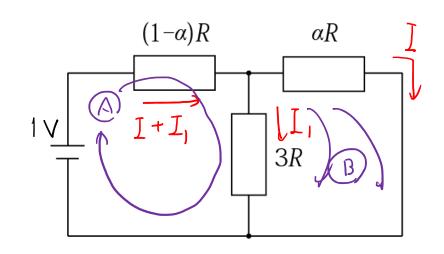
$$\alpha = \frac{1}{2} / \sqrt{\frac{1}{2}}$$




(2) 統統行列


$$\begin{pmatrix} 1 \\ I_1 \end{pmatrix} = \begin{pmatrix} 1 & (1-\alpha)R \\ D & 1 \end{pmatrix} \begin{pmatrix} 1 & D \\ \frac{1}{3R} & 1 \end{pmatrix} \begin{pmatrix} 0 \\ D & 1 \end{pmatrix} \begin{pmatrix} 1 & \alpha \\ 0 & 1 \end{pmatrix} \begin{pmatrix} 0 \\ 1 & \alpha \end{pmatrix}$$

$$= \begin{pmatrix} \frac{4}{3} - \frac{d}{3} & (1-\alpha)R \\ \frac{1}{3R} & 1 \end{pmatrix} \begin{pmatrix} \alpha RI \\ I \end{pmatrix}$$

$$= \begin{pmatrix} \frac{4}{3}\alpha - \frac{d^2}{3} + 1 - \alpha \end{pmatrix} RI$$
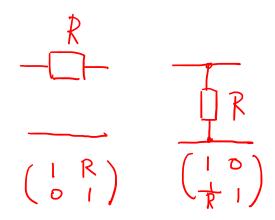
$$= \begin{pmatrix} \frac{d}{3}\alpha - \frac{d^2}{3} + 1 - \alpha \end{pmatrix} RI$$




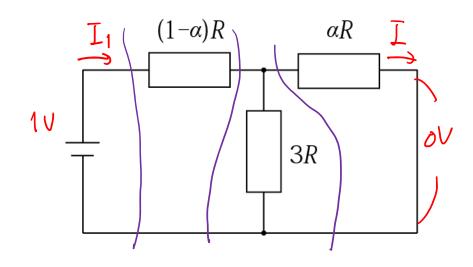


(3) デブナンタ定理

$$E = 1 \times \frac{3R}{(4-\alpha)R} = \frac{3}{4-\alpha}$$

$$(1-\alpha)R + 3R$$

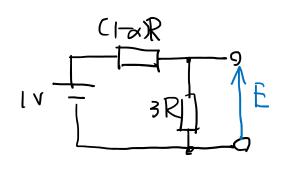


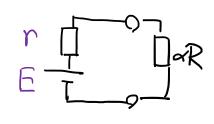

$$\frac{1}{r} = \frac{1}{(1-\alpha)R} + \frac{1}{3R} = \frac{4-\alpha}{3(1-\alpha)R}$$

$$r = \frac{3(1-\alpha)}{4-\alpha} R$$
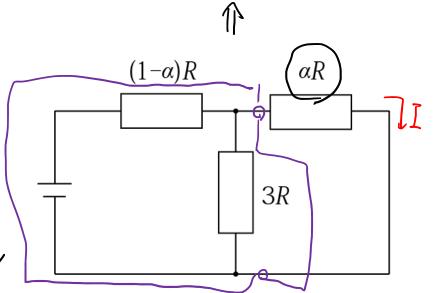
$$= \sum_{r + \alpha R} = \frac{\frac{3}{4-\alpha}}{\frac{3(1-\alpha)}{4-\alpha} + \alpha} R = \frac{3}{(-\alpha^2 + \alpha + 3)R}$$



(4) 電压振的電流源

$$I : I_{1} : I_{2} = \frac{1}{\alpha} : \frac{1}{3} : \frac{1}{1-\alpha}$$

$$I_{r} = E = \frac{1}{3} : \frac{1}{1-\alpha}$$

$$I_{r} = \frac{1}{3} : \frac{1}{1-\alpha}$$

$$I_{r} = \frac{1}{3} : \frac{1}{3} : \frac{1}{1-\alpha}$$

$$I_{r} = \frac{1}{3} : \frac{1}{3} : \frac{1}{1-\alpha}$$

$$I_{r} = \frac{1}{3} : \frac{1}$$